

**INSTITUTE OF TEXTILE TECHNOLOGY**



**INDUSTRIAL ELECTRONICS LAB  
MANNUAL**

**BRANCH- MECHATRONICS ENGG.**

**5<sup>TH</sup> SEMESTER**

**EXPERIMENT – 1(A)**  
**STUDY OF CHARACTERISTICS OF SCR, MOSFET & IGBT**

**SCR CHARACTERISTICS**


**AIM:**

To plot the V - I Characteristics of SCR, MOSFET & IGBT.


**APPARATUS:**

S. No	Equipment	Range	Type	Quantity
1	SCR characteristics Trainer	-	-	1
2	Patch chords	-	-	
3	DC Voltmeter	-	Digital	1
4	DC Ammeter	-	Digital	1

**CIRCUIT DIAGRAM:**

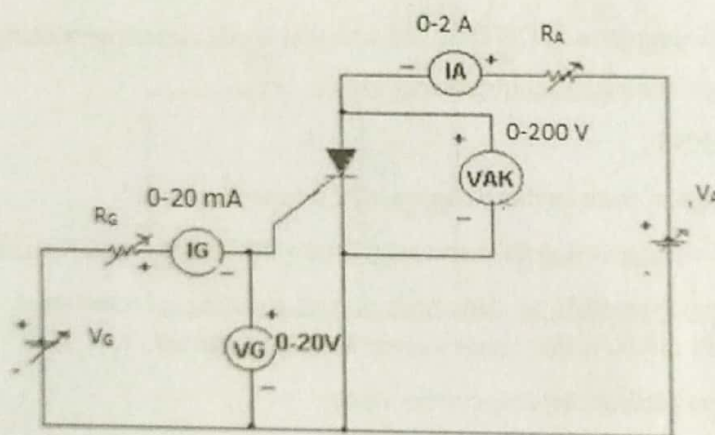

**Symbol**

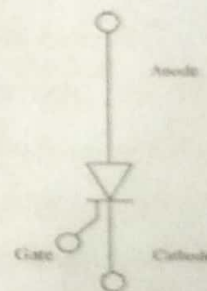

**Study of Characteristics of SCR**

**PROCEDURE:**

**V - I CHARACTERISTICS:**

1. Make all connections as per the circuit diagram.
2. Initially keep  $V_G$  &  $V_A$  at minimum position and  $R_1$  &  $R_2$  maximum position.
3. Adjust Gate current  $I_g$  to some constant by varying the  $V_G$  or  $R_G$ .
4. Now slowly vary  $V_A$  and observe Anode to Cathode voltage  $V_{AK}$  and Anode current  $I_A$ .
5. Tabulate the readings of Anode to Cathode voltage  $V_{AK}$  and Anode current  $I_A$ .
6. Repeat the above procedure for different Gate current  $I_g$ .

**GATE TRIGGERING AND FINDING  $V_G$  AND  $I_G$ :**

1. Keep all positions at minimum.



2. Set Anode to Cathode voltage  $V_{AK}$  to some volts say 15V.
3. Now slowly vary the  $V_G$  voltage till the SCR triggers and note down the reading of gate current ( $I_G$ ) and Gate Cathode voltage ( $V_{GK}$ ) and rise of anode current  $I_A$ .
4. Repeat the same for different Anode to Cathode voltage and find  $V_{AK}$  and  $I_G$  values.

#### TO FIND LATCHING CURRENT:

1. Keep  $R_2$  at middle position.
2. Apply 20V to the Anode to cathode by varying  $V_2$ .
3. Rise the  $V_g$  voltage by varying  $V_G$  till the device turns ON indicated by sudden rise in  $I_A$ .  
At what current SCR trigger it is the minimum gate current required to turn ON the SCR.
4. Now set  $R_A$  at maximum position, then SCR turns OFF, if it is not turned off reduce  $V_A$  up to turn off the device and put the gate voltage.
5. Now decrease the  $R_A$  slowly, to increase the Anode current gradually in steps.
6. At each and every step, put OFF and ON the gate voltage switches  $V_G$ . If the Anode current is greater than the latching current of the device, the device stays ON even after switch OFF  $S_1$ , otherwise device goes to blocking mode as soon as the gate switch is put OFF.
7. If  $I_A > I_L$  then, the device remains in ON state and note that anode current as latching current.
8. Take small steps to get accurate latching current value.

#### TO FIND HOLDING CURRENT:

1. Now increase load current from latching current level by varying  $R_A$  &  $V_A$ .
2. Switch OFF the gate voltage switch  $S_1$  permanently (now the device is in ON state).
3. Now increase load resistance ( $R_2$ ), so that anode current reducing, at some anode current the device goes to turn off. Note that anode current as holding current.
4. Take small steps to get accurate holding current value.
5. Observe that  $I_H < I_L$ .

#### TABULAR COLUMN:

S. No	$I_G =$ Amps	
	$V_{AK}$ (Volts)	$I_A$ (Amps)
1		
2		
3		
4		
5		

S. No	$I_G =$ Amps	
	$V_{AK}$ (Volts)	$I_A$ (Amps)
1		
2		
3		
4		
5		

## EXPERIMENT – 1(B) MOSFET CHARACTERISTICS


### AIM:

To study the output and transfer characteristics of MOSFET

### APPARATUS:

S. No	Equipment	Range	Type	Quantity
1	MOSFET characteristics Trainer			
2	Patch chords			
3	DC Voltmeter			
4	DC Ammeter			

### CIRCUIT DIAGRAM:

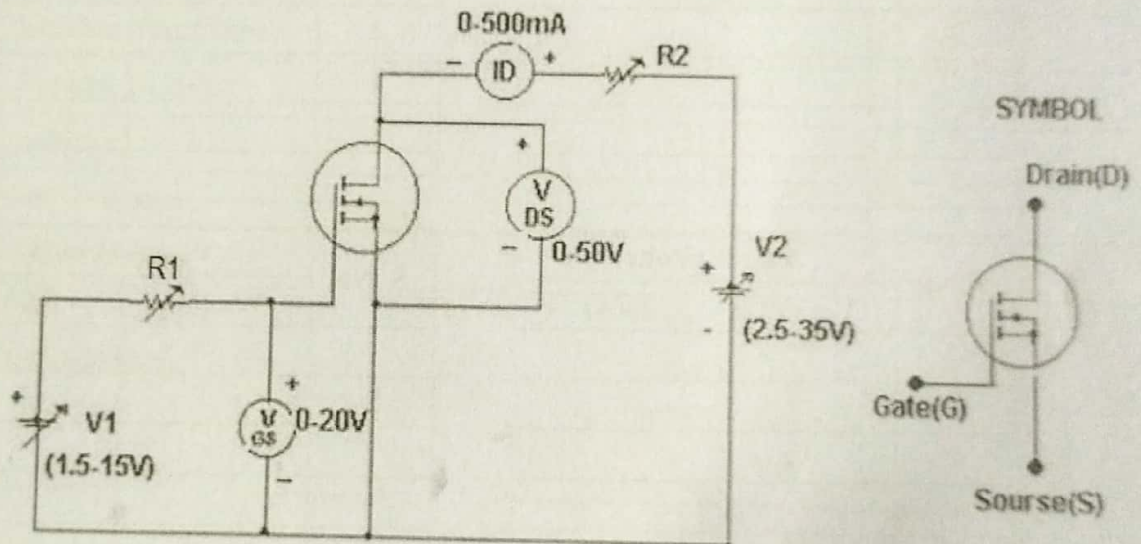

### Study of Characteristics of MOSFET

#### PROCEDURE:

#### TRANSFER CHARACTERISTICS:

1. Make all connections as per the circuit diagram.
2. Initially keep  $V_1$  &  $V_2$  at minimum position and  $R_1$  &  $R_2$  middle position.
3. Set  $V_{DS}$  to some say 10V.
4. Slowly vary Gate source voltage  $V_{GS}$  by varying  $V_1$ .
5. Note down  $I_D$  and  $V_{GS}$  readings for each step.
6. Repeat above procedure for 20V & 30V of  $V_{DS}$ . Draw Graph between  $I_D$  &  $V_{GS}$ .



## OUTPUT CHARACTERISTICS:

1. Initially set  $V_{GS}$  to some value say 3V by varying  $V_1$ .
2. Slowly vary  $V_2$  and note down  $I_D$  and  $V_{DS}$ .
3. At particular value of  $V_{GS}$  there a pinch off voltage between drain and source.  
If  $V_{DS} < V_P$  device works in the constant resistance region and  $I_D$  is directly proportional to  $V_{DS}$ . If  $V_{DS} > V_P$  device works in the constant current region.
4. Repeat above procedure for different values of  $V_{GS}$  and draw graph between  $I_D$  vs  $V_{DS}$ .

## TABULAR COLUMN:


S. No.	$V_{GS} =$ VOLTS	
	$V_{DS}$ (Volts)	$I_D$ (Amps)
1		
2		
3		
4		
5		

S. No	$V_{GS} =$ VOLTS	
	$V_{DS}$ (Volts)	$I_D$ (Amps)
1		
2		
3		
4		
5		


S. No	$V_{DS} =$ (Volts)	
	$V_{GS}$ (V)	$I_D$ (A)
1		
2		
3		
4		
5		

S. No	$V_{DS} =$ (Volts)	
	$V_{GS}$ (V)	$I_D$ (A)
1		
2		
3		
4		
5		

## MODEL GRAPH:

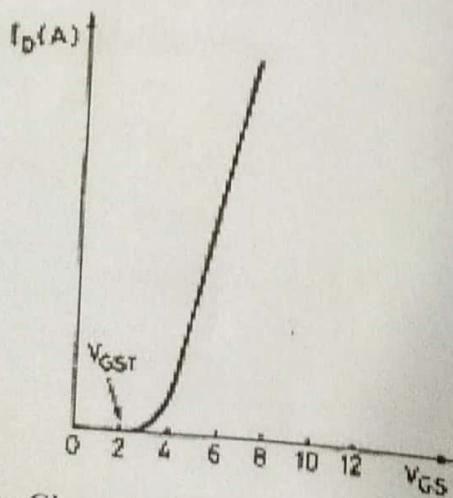

Transfer Characteristic of MOSFET

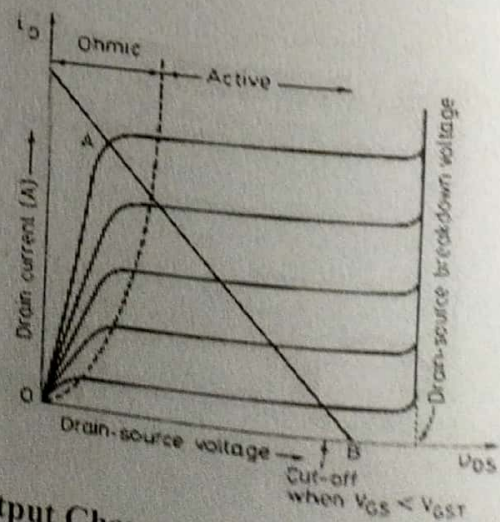

Output Characteristics of MOSFET



### EXPERIMENT - 3

## SINGLE PHASE FULLY CONTROLLED BRIDGE CONVERTER WITH R AND RL LOADS


#### AIM:

To study the single phase fully controlled bridge converter with R & RL Load.

#### APPARATUS:

S. No	Equipment	Range	Type	Quantity
1	Single phase full controlled bridge converter power circuit and firing circuit			
2	CRO with deferential MODEL			
3	Patch chords and probes			
4	Isolation Transformer			
5	Variable Rheostat			
6	Inductor			
7	DC Voltmeter			
8	DC Ammeter			

#### CIRCUIT DIAGRAM:

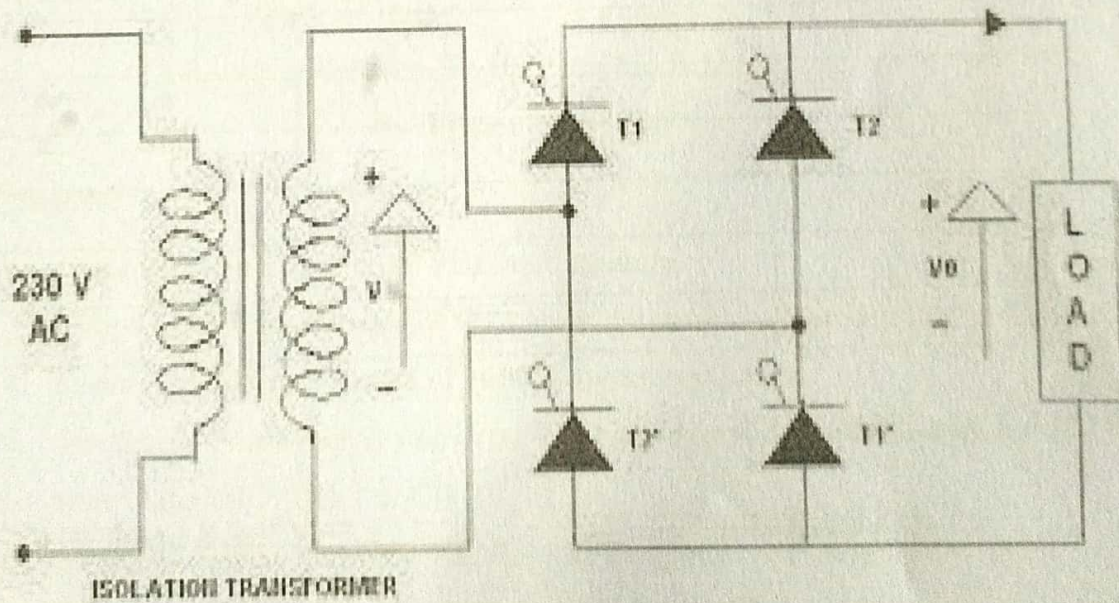

Single Phase Fully Controlled Bridge Converter

**PROCEDURE:**

1. Make all connections as per the circuit diagram
2. Connect firstly 30V AC supply from Isolation Transformer to circuit.
3. Connect firing pulses from firing circuit to Thyristors as indication in circuit.
4. Connect resistive load 200Ω / 5A to load terminals and switch ON the MCB and IRS switch and trigger output ON switch.
5. Connect CRO probes and observe waveforms in CRO across load and device in single phase fully controlled bridge converter.
6. By varying firing angle gradually up to 180° and observe related waveforms.
7. Measure output voltage and current by connecting AC voltmeter & Ammeter.
8. Tabulate all readings for various firing angles.
9. For RL Load connect a large inductance load in series with Resistance and observe all waveforms and readings as same as above.
10. Observe the various waveforms at different points in circuit by varying the Resistive Load and Inductive Load.
11. Calculate the output voltage and current by theoretically and compare with it practically obtained values.

**TABULAR COLUMN:**

S. No	Input Voltage (V <sub>in</sub> )	Firing angle in Degrees	Output voltage (V <sub>o</sub> )		Output Current (I <sub>o</sub> )	
			Theoretical	Practical	Theoretical	Practical
1						
2						
3						
4						
5						
6						

**MODEL CALCULATIONS:**

For R-L Load:

$$V_o = (2\sqrt{2}V/\pi) * \cos \alpha$$

$$I_o = (2\sqrt{2}V/\pi R) * \cos \alpha$$

$\alpha$  = Firing Angle

V = RMS Value across transformer output

For R Load:

$$V_o = (\sqrt{2}V/\pi) * (1 + \cos \alpha)$$

$$I_o = (\sqrt{2}V/\pi R) * (1 + \cos \alpha)$$



## EXPERIMENT - 04

### GATE FIRING CIRCUITS FOR SCRS (R - C TRIGGERING)


#### AIM:

To study the Resistance - capacitance (RC) Triggering circuit of SCR.

#### APPARATUS:

S. No	Name of the Equipment	Range	Qty
1	Resistance-Capacitance Firing Circuit		
2	Patch chords		
3	CRO with differential MODEL		
4	R-Load		

#### CIRCUIT DIAGRAM:

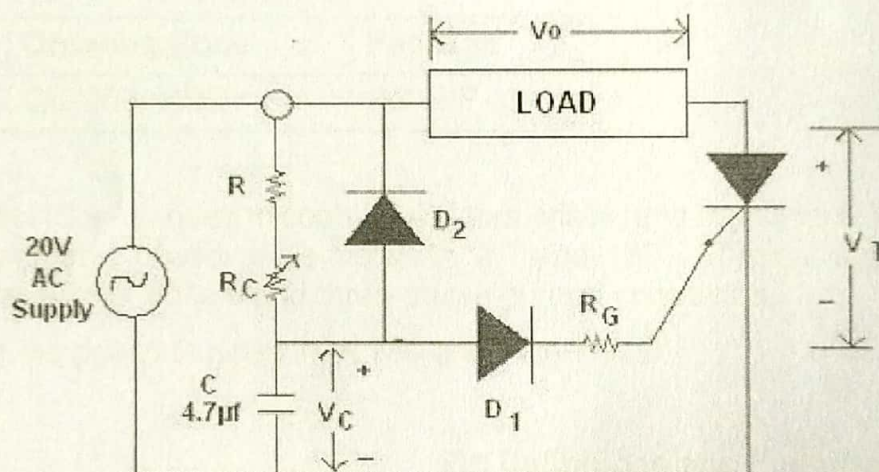


RC Triggering Circuit

#### PROCEDURE:


1. Make all connections as per the circuit diagram.
2. Give the AC Power supply 20V/1A from the source indicated in the front panel.
3. Connect Load i.e., Rheostat of  $200\Omega$  between two points.
4. Switch ON Power supply and observe the wave forms of input & output at a time in the CRO.[CH-1 or CH-2].
5. Slowly vary the control Resistor  $R_C$ , that firing angle can vary from  $0-180^\circ$ .
6. Observe various voltage waveforms across load, SCR and other points, by varying the Load Resistance and Firing  $R_C$  part.
7. Compare practical obtained voltage waveform with theoretical waveform and observe the Firing angle in R - C Triggering.



MODEL GRAPH:

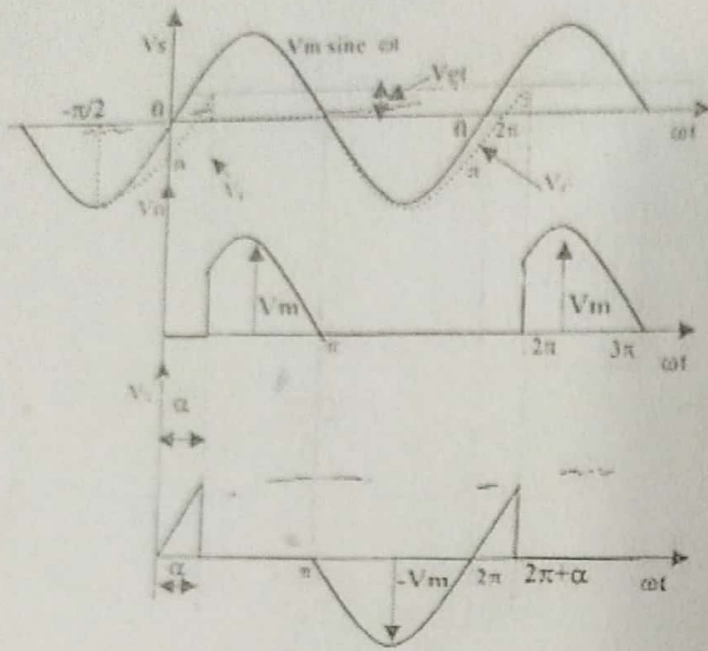


For Small Value of R

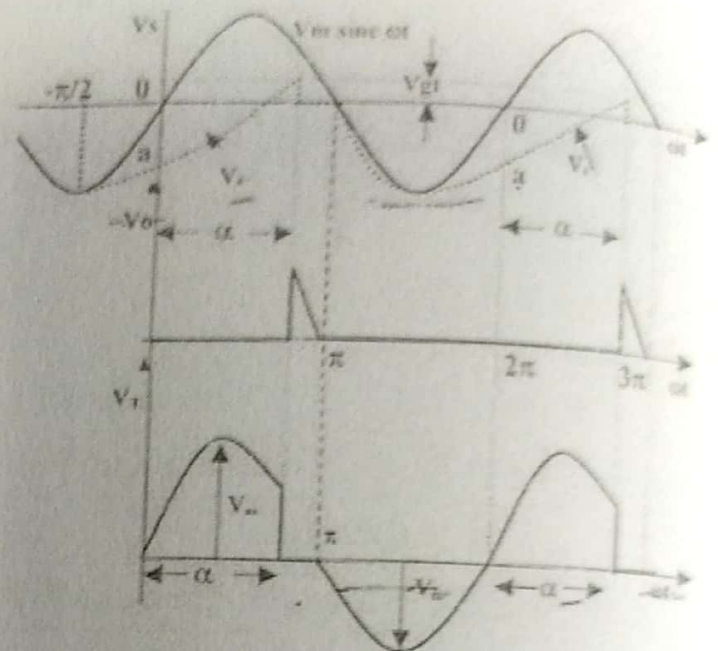

For Large Value of R

Output Wave forms of RC Triggering

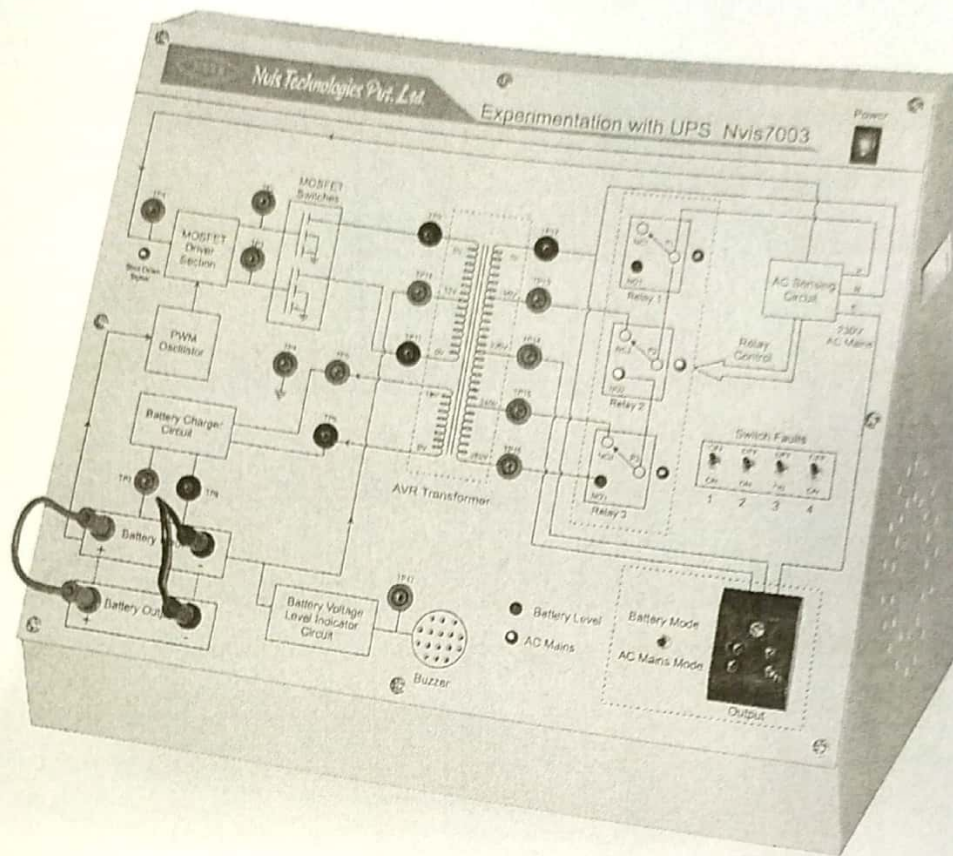

**Nvis 7003 Experimentation with UPS** is a very versatile training system, has been designed to explain a very interesting and frequently used switching based power supply-The UPS (Uninterrupted Power Supply).

When electrical utility power fails or drops to an unacceptable level, UPS are key in saving and protecting valuable computer data. UPS equipment provides power conditioning, power regulation and, in case of power outages, provides the crucial backup power needed for an orderly shutdown of computer processes and files. UPS are also used for emergency power supplies for Hospitals, data centers, municipalities, industrial and commercial centers to supply power in case of power failure from main supply authority.

## Features

- In depth explanation of PWM switching technology, which is one of the most important feature of UPS
- A Low cost product demonstrating all basic concept of UPS
- Various test point are provided so that one can easily measure the voltages of different sections
- Designed considering all safety standards
- Online product tutorial



## Scope of Learning

- Study of PWM Technology
- To understand the overall functioning of UPS Trainer
- Study of AVR transformer section of UPS
- To study the UPS circuit in load condition
- To identify different faults and to study the systematic procedure of their troubleshooting in UPS circuit

## Technical Specifications

**Input Voltage** : 190 to 260V AC  $\pm 10\%$ , 50Hz  
(Single Phase)

**Output Voltage** : 230V AC,  $\pm 10\%$

### Transformer

**Input** : 12-0-12V AC

**Outputs** : 0, 190, 220, 240, 260V AC  
18-0V AC for battery charging

### Battery

**Rating** : 12V DC / 7.5 AH

**Type** : SMF Rechargeable Battery

**Technology** : MOSFET-PWM

**Output Power Capacity** : 500VA

**Dimensions (mm)** : W 365 x D 260 x H 120

**Weight** : 5kg (approximate)

### Optional

Oscilloscope 'Caddo 801'

Multimeter 'Caddo 50/51'